 


Combinational Circuits.

2 classes of logic circuits


1. Combinational

each output depends entirely on the immediate (present) inputs.




 2. Sequential

each output depends on both present inputs and state.



Circuit analysis

 

Steps:

1. Label the inputs and outputs.
2. Obtain the functions of intermediate points and the outputs.
3. Draw the truth table:

A	B	$(A+B)$	$(A'+B')$	F1	F2
0	0	0	1	0	0
0	1	1	1	1	0
1	0	1	1	1	0
1	1	1	0	0	1

Sum Carry

4. Deduce the functionality of the circuit

⇒ Half adder

Circuit Design.

- Gate-level design method (w/ logic gates) → available as integrated circuit chips.
- Block-level design method (w/ functional blocks) →


- Main Objective: reduce cost / no. of gate / no. of IC,
increase speed,
design simplicity (re-usable blocks)

eg. Design Half Adder.

Design procedure:

1. State problem Build a Half Adder

 2. Determine the inputs and outputs of the circuit.



3. Draw the truth table

X	Y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

4. Obtain simplified Boolean functions


eg.

$$C = X \cdot Y$$



$$S = X' \cdot Y + X \cdot Y'$$

$$= X \oplus Y$$

5. Draw the logic Half Adder.

 

other ways:

  


eg. Design Full Adder

- Half adder adds up only 2 bits
- To add 2 binary numbers, we need to add 3 bits (including the carry).

ie.

$$\begin{array}{r}
 \begin{array}{cccc} 1 & 1 & 1 & 0 \end{array} \quad \text{carry} \\
 \begin{array}{cccc} 0 & 0 & 1 & 1 \end{array} \quad X \\
 + \begin{array}{cccc} 0 & 1 & 1 & 1 \end{array} \quad Y \\
 \hline
 \begin{array}{cccc} 1 & 0 & 1 & 0 \end{array} \quad S
 \end{array}$$

 - Need **Full Adder** (can be made from 2 half adders)



- Truth Table.

X	Y	Z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Note:

Z - carry in (to the current position)

C - carry out (to the next position)

- K-map

X\YZ	00	01	11	10
0	0	0	1	0
1	0	1	1	1

X\YZ	00	01	11	10
0	0	1	0	1
1	1	0	1	0

- Simplified SOP form:

$$C = X \cdot Y + X \cdot Z + Y \cdot Z$$

$$S = X' \cdot Y' \cdot Z + X' \cdot Y \cdot Z' + X \cdot Y' \cdot Z' + X \cdot Y \cdot Z$$

↓ Simplify \approx NOR

$$\begin{aligned}
 C &= X \cdot Y + X \cdot Z + Y \cdot Z \\
 &= X \cdot Y + (X + Y) \cdot Z \\
 &= X \cdot Y + ((X \oplus Y) + X \cdot Y) \cdot Z \\
 &= X \cdot Y + (X \oplus Y) \cdot Z + X \cdot Y \cdot Z \\
 &= X \cdot Y + (X \oplus Y) \cdot Z
 \end{aligned}$$


$$\begin{aligned}
 X + Y &= (X \oplus Y) + X \cdot Y \\
 X \oplus Y &= X' \cdot Y + X \cdot Y' \\
 (X \oplus Y) + X \cdot Y &= X' \cdot Y + X \cdot Y' + X \cdot Y \\
 &= X' \cdot Y + X \cdot Y' + X \cdot Y + X \cdot Y \\
 &= (X' + X) \cdot Y + X \cdot (Y' + Y) \\
 &= Y + X
 \end{aligned}$$

$$\begin{aligned}
 S &= X' \cdot Y' \cdot Z + X' \cdot Y \cdot Z' + X \cdot Y' \cdot Z' + X \cdot Y \cdot Z \\
 &= X' \cdot (Y' \cdot Z + Y \cdot Z') + X \cdot (Y' \cdot Z' + Y \cdot Z) \\
 &= X' \cdot (Y \oplus Z) + X \cdot (Y \oplus Z)' \\
 &= X \oplus (Y \oplus Z)
 \end{aligned}$$


Circuit Implementation

$$C = X \cdot Y + (X \oplus Y) \cdot Z$$
 
$$\begin{aligned}
 S &= X \oplus (Y \oplus Z) \\
 &= (X \oplus Y) \oplus Z
 \end{aligned}$$



made from 2 Half-Adders
(+ an OR gate)

 


Block Diagrams.

• Code converter

• takes an input code, translates to its equivalent output code.

• i.e.

 


• eg. BCD to excess-3 code converter

Binary Coded Decimal

Input: BCD code

Output: Excess-3 code.

Digit	BCD code	Excess-3 code
0	0000	0011
1	0001	0100
2	0010	0101
3	0011	0110
4	0100	0111
5	0101	1000
6	0110	1001
7	0111	1010
8	1000	1011
9	1001	1100

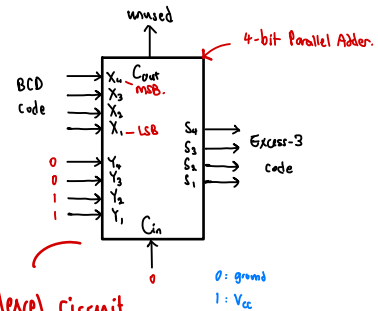

∴ 4 variable truth table


output = input + 3.

invalid since decimal is from 0-9.

	BCD				Excess-3			
	A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	0	1	1
1	0	0	0	1	0	1	0	0
2	0	0	1	0	0	1	0	1
3	0	0	1	1	0	1	1	0
4	0	1	0	0	0	1	1	1
5	0	1	0	1	1	0	0	0
6	0	1	1	0	1	0	0	1
7	0	1	1	1	1	0	1	0
8	1	0	0	0	1	0	1	1
9	1	0	0	1	1	1	0	0
10	1	0	1	0	X	X	X	X
11	1	0	1	1	X	X	X	X
12	1	1	0	0	X	X	X	X
13	1	1	0	1	X	X	X	X
14	1	1	1	0	X	X	X	X
15	1	1	1	1	X	X	X	X

⇒

K-maps

 

∴ Simplified boolean expression :

$$W = A + B \cdot C + B \cdot D$$

$$X = B' \cdot C + B' \cdot D + B \cdot C' \cdot D'$$

$$Y = C \cdot D + C' \cdot D$$

$$Z = D'$$

Block-Level Design


- More complex circuits can also be built using **block-level** methods.
- In-general, block-level design method (as opposed to gate-level design) relies on **algorithms or formulae** of the circuit, which are obtained by decomposing the main problem to sub-problems recursively (until small enough to be directly solved by blocks of circuits)

- eg. Using **4-bit parallel adders** as building blocks, we can create the following:

 1. BCD-to-Excess-3 Code Converter.
2. 16-bit Parallel Adder.

4-bit parallel adder

- add 2 4-bit numbers together and carry-in, to produce a 5-bit result.



- 5-bit result is sufficient** because the largest result is:

$$1111_2 + 1111_2 + 1_2 = 11111_2.$$

- Gate-level design should not be used here!

⇒ truth table for 9 inputs is too big: $2^9 = 512$ rows!

- Alternative design possible

- Addition formula for pair of bits (w/ carry in)


$$C_{i+1} S_i = X_i + Y_i + C_i$$

has the same function as a **full adder**:

$$C_{i+1} = X_i \cdot Y_i + C X_i \oplus Y_i \cdot C_i$$

$$S_i = X_i \oplus Y_i \oplus C_i$$

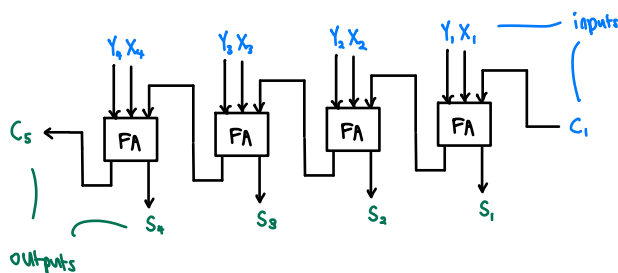
- ∴ each full adder handles one column of addition:



- Carry is propagated by cascading the carry from one full adder to the next.
- Parallel** Adder because the inputs are presented simultaneously (in parallel) (also called the **Ripple-Carry Adder**)

16-bit Parallel Adder?

 - Larger parallel adders can be built from smaller ones
- eg.



Magnitude Comparator


- Compares 2 unsigned values A and B, checks if $A > B$, $A = B$, $A < B$.
- An n-bit magnitude comparator using classical method requires 2^{2n} rows in truth table.
- Exploit **regularity** in design
- Compare 2 4-bit unsigned values

$A(a_3a_2a_1a_0)$ and $B(b_3b_2b_1b_0)$

• If $a_3 > b_3$, then $A > B$.


• If $a_3 < b_3$, then $A < B$.

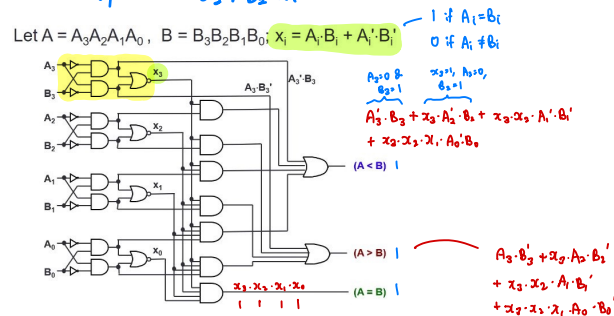• If $a_3 = b_3$, then if $a_2 > b_2 \dots$



...

 
Block diagram of 4-bit magnitude comparator



Circuit Delays


- each logic gate have a certain delay.
- given a logic gate with delay t , if inputs are stable at times t_1, t_2, \dots, t_n , then the earliest time in which the output will be stable is:

$$\max(t_1, t_2, \dots, t_n) + t.$$

 


Delay of all outputs of a combinational circuit, repeat the above rule for all gates.

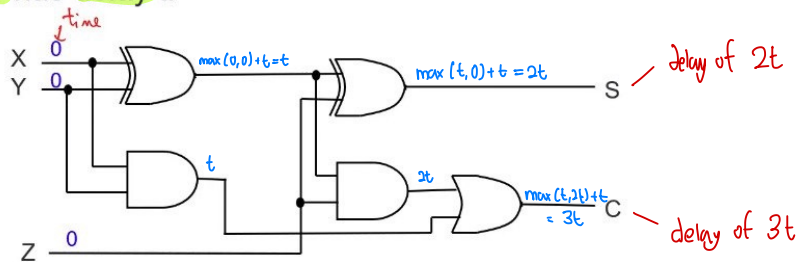
As a simple example, consider the full adder circuit where all inputs are available at time 0. Assume each gate has delay t .



More complex example:

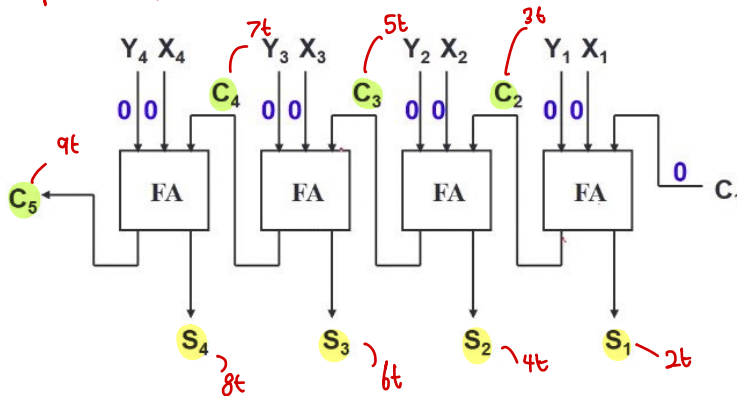


 - Analyse the delay for the repeated block.



In general, an n -bit ripple-carry parallel adder will experience the following delay times:

- Performing the delay calculation:

 


$$S_n = ((n-1)2+2)t$$

$$C_{n+1} = ((n-1)2+3)t$$

propagation delay of ripple-carry parallel adder is proportional to the no. of bits it handles.

The circuit is a 2-bit adder-cum-subtractor. If C_{in} is set to 0, it performs $X + Y$. If C_{in} is 1, it performs $X - Y$.

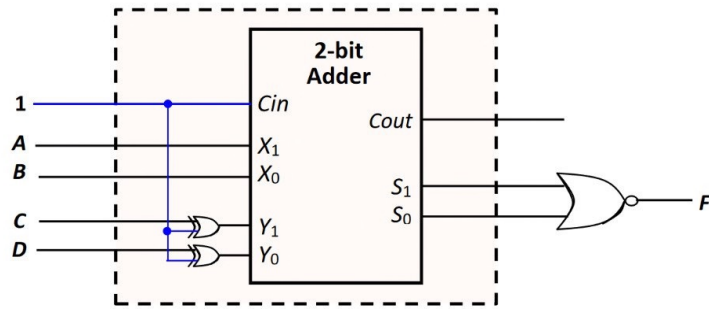Since $F=1$ when $AB = CD$, or $AB - CD = 0$, the solution is shown below. (Other answers possible).



Half-adder \equiv or