#### NATIONAL UNIVERSITY OF SINGAPORE

#### **CS2100 – COMPUTER ORGANISATION**

(Semester 2: AY2017/18)

# **ANSWER BOOKLET**

Time Allowed: 2 Hours

## **INSTRUCTIONS TO CANDIDATES**

- 1. This answer booklet consists of SIX (6) printed pages.
- 2. Fill in your Student Number with a pen clearly below. Do NOT write your name.
- 3. You may write your answers in pencil (2B or above).

STUDENT NUMBER (fill in with a pen):

Α	0	1						
---	---	---	--	--	--	--	--	--

For examiner's use only						
Question	Total	Marks				
Q1	10					
Q2	15					
Q3	20					
Q4	12					
Q5	15					
Q6	14					
Q7	14					
Total	100					

### CS2100

Write your answers in the box/space provided.


1a. [4] 1b. [3]

1c.
[3] F =Circuit delay =


Q1: /10

Q2: /15




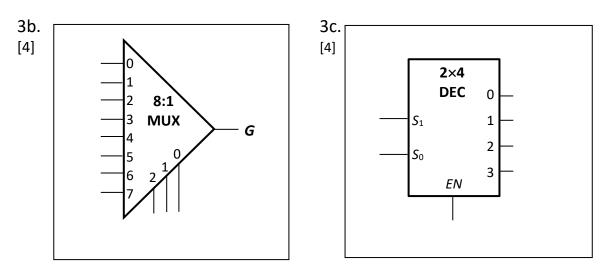


3d.													_
[8]		A	4					-	A				
	<i>A</i> <sub>3</sub>	$A_2$	$A_1$	$A_0$	128	64	JJ	16 2	×A &	+	J	ſ	
ð	0	0	0	0	0	0	C	0	0	0	0	0	
1	0	0	0	1	0	0	0	O	0	(	Ð	\	
2	0	0	1	0	0	2	0	C	(	0	1	0	X
3	0	0	1	1	0	5	0	0	1	Ţ	\	\	X
Y	0	1	0	0	0	0	0	ı	0	ſ	Ð	0	
5	0	1	0	1	0	0	0			·(~	0	\	
6	0	1	1	0	C	0	٥	1		1	ľ	0	
7	0	1	1	1	C	0	1	0	O	. С	1	)	
8	1	0	0	0	0	O	1	0		0	0	0	
9	1	0	0	1	0	0	1	0	\	0		Ĭ	

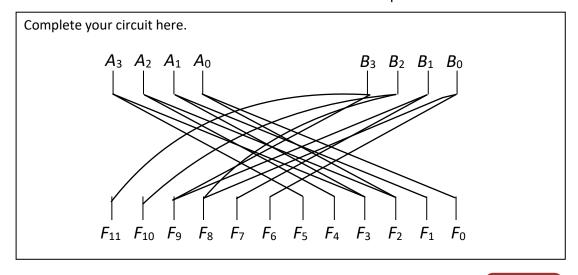

4a.	
[2]	Maximum total instructions =

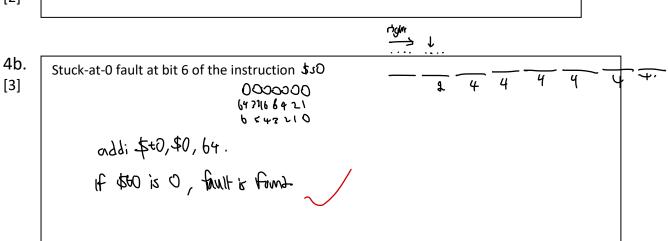

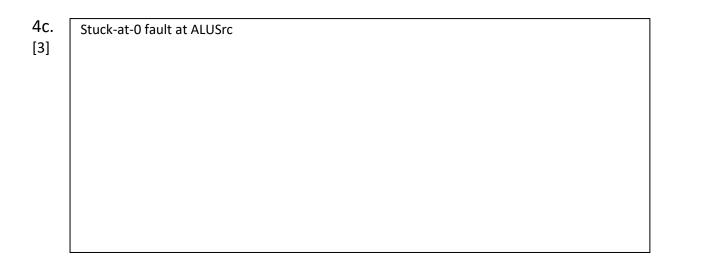

4d. [4]	Adding bne instruction

Q4: /12

5a. [1]					
5b. [4]	Array A:				
5c. [4]					
5d. [2]		5e. [2]		5f. [2] Q5:	/15
6a. [ [2]	Minimum = Maximum =				
6b. [6]					
6c. [ [3]	cycles	6d. [3]	cycles	Q6:	/14

### CS2100

7a. [ [2]	Index: bits;	Offset: bits
7b. [	A[1023] → Index;	<i>B</i> [1023] → Index;
7c. [ [2]	Array A: accesses;	Array B: accesses
7d. [ [2]	Array <i>A</i> : %;	Array <i>B</i> : %
7e. [ [4]	Misses:;	Hits:

Q7:	/14

=== END OF PAPER ===